



# PRESIDENCY COLLEGE

(AUTONOMOUS)

AFFILIATED TO BENGALURU CITY UNIVERSITY, APPROVED BY AICTE, DELHI & RECOGNISED BY THE GOVT. OF KARNATAKA  
RE-ACCREDITED BY NAAC WITH 'A+' GRADE

## II Semester BCA Mid Term Re Examination May 2022 GC206.2C: COMPUTER ARCHITECTURE

Date: 30.06.2022

Duration: 1 ½ Hours

Max Marks: 40

*Instruction: Answers should be written in English only.*

### PART- A

Answer any SIX questions. Each question carries TWO marks.

(6 X 2=12)

1. Convert  $(13)_{10}$  to  $(?)_2$
2. Draw the logic diagram and truth table of OR gate
3. What is toggling and race condition?
4. What is combinational circuit? Give examples
5. Find 1's complement and 2's complement of 10001
6. Write any two differences between encoder and decoder.
7. How IC'S are classified?
8. Write the basic instruction format.

### PART-B

Answer any THREE questions. Each question carries SIX marks.

(3 X 6=18)

1. Simplify using K-Map  $F(A, B, C, D) = \sum m(0, 1, 2, 5, 7, 8, 9, 10, 13, 15)$
2. What is full adder? Explain with circuit diagram and truth table.
3. What is encoder? Explain encoder with truth table and diagram.
4. Draw the flowchart of instruction cycle.
5. Explain the various instruction formats.

### PART-C

Answer any ONE question. Each question carries TEN marks.

(1 X 10=10)

1. What is flip flop? Explain SR Flip flop with diagram and state table.

2. What are sequential circuits? Construct sequential circuit for:

Input Equation:

$$D_A = Ax + Bx$$

$$D_B = A'x$$

Output Equation:

$$Y = Ax' + Bx'$$

Write the state table and state diagram for the same

\*\*\*\*\*